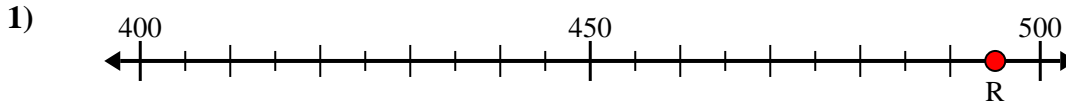





Encontrar el valor de R.


Respuestas




1. _____

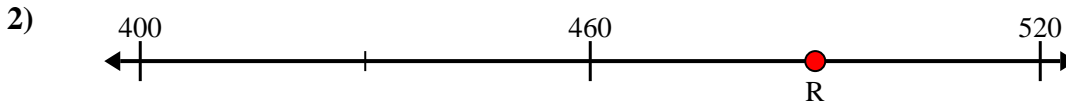


2. _____

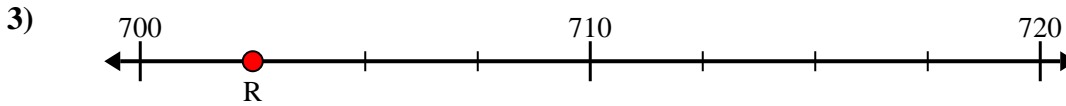


3. _____

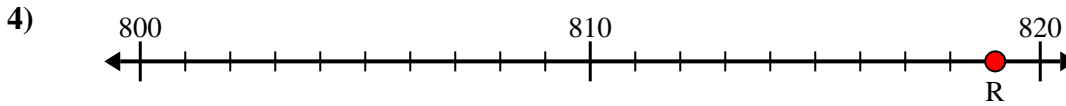


4. _____

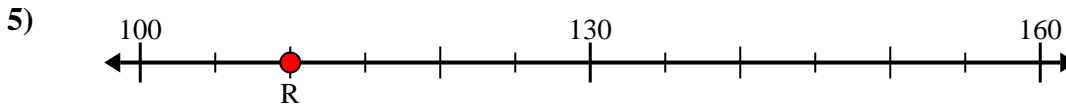


5. _____

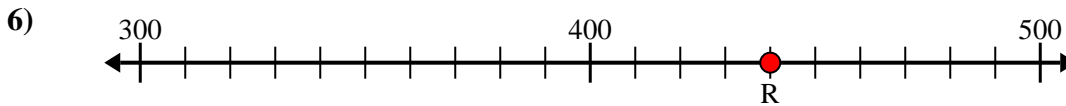


6. _____

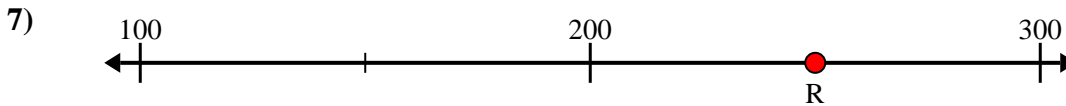


7. _____

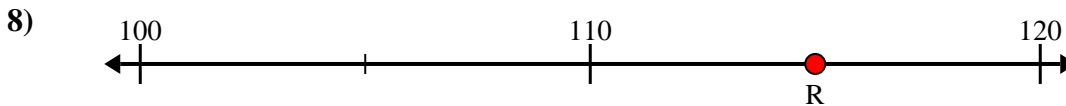

8. _____

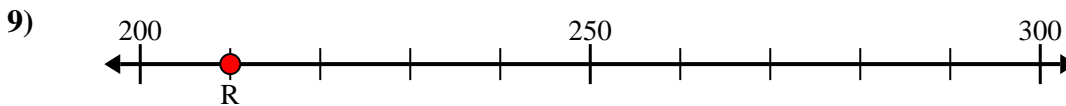

9. _____










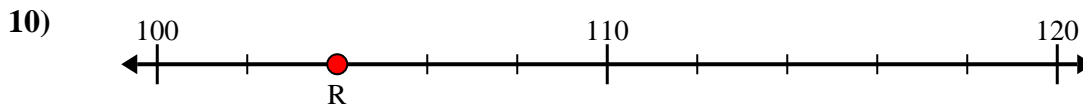


10. _____

10. _____



Encontrar el valor de R.

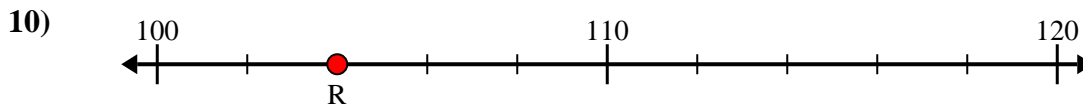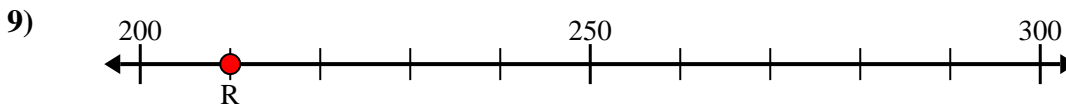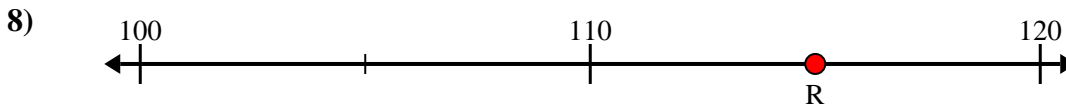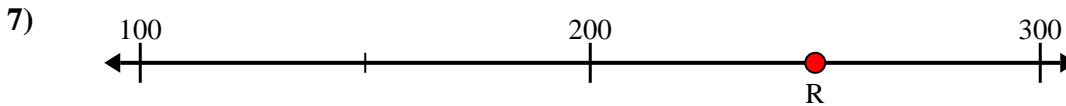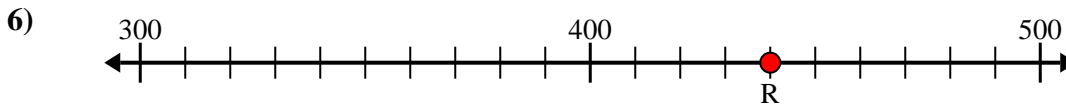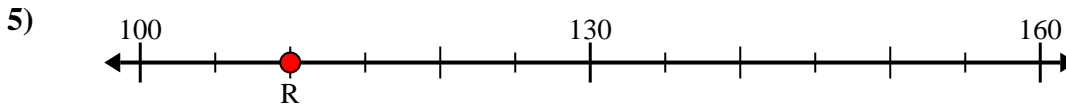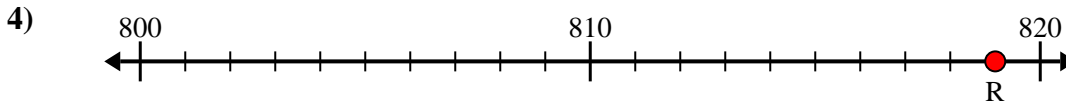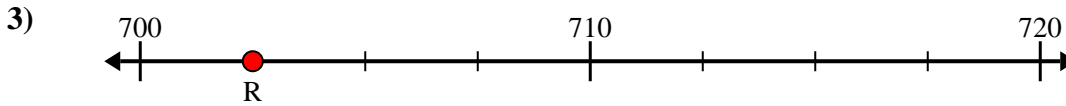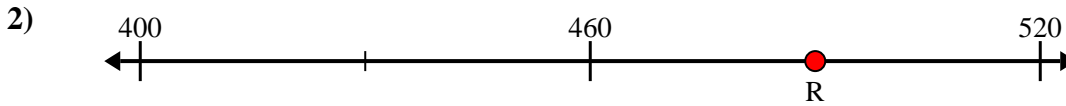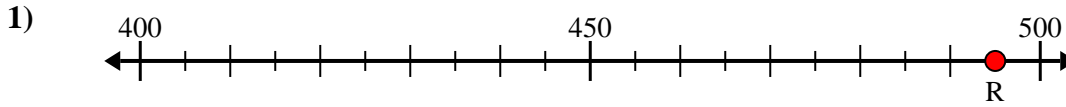

Respuestas

1. 495

2. 490

3. 702.5

4. 819

5. 110

6. 440

7. 250

8. 115

9. 210

10. 104